

Assignment 3

Part 1: testbenches

Remarks:


- it is advised that the testbenches are a mix of randomization and directed testing with realistic inputs, to check for full functionality.
- Apply self-checking task for at least one of the designs below.

Q1) Using the ALU (Arithmetic Logic Unit) designed in assignment 2, use Verilog to create a testbench for this design to test the functionality of the design.

The testbench should include at least 100 testcases.

Q2) Design and test the following D-latch.

Input	Output
D	Q
en	-

 

Truth Table		
En	D	Q
0	X	0
1	D	D

Make sure to create a testbench for this design with at least 100 test cases.

Part 2: Sequential

Q3) Design a Flip-Flop module that can function as either a D Flip-Flop or a T Flip-Flop based on a parameter FF_TYPE.

- If FF_TYPE = DFF: The module should behave as a D Flip-Flop.
- If FF_TYPE = TFF: The module should behave as a T Flip-Flop.
- The Flip-Flop should have an **active-low reset (rst_n)**.
- The module should **provide both Q and Qbar** (complement of Q) as outputs.
- Parameters:
 1. FF_TYPE: default value = "DFF"
- Inputs:
 1. clk: Clock signal.
 2. rst_n: Active-low reset
 3. D: Data input
- Outputs:
 1. Q: Flip-Flop output.
 2. Qbar: Complement of Q.

Q4) Draw the schematic for the following Verilog designs

```
module reg_blocking1 (  
    input clk, rst, in,  
    output reg out  
);  
    reg q, q2;  
    always @(posedge clk) begin  
        if (rst) begin  
            q2 = 0;  
            q1 = 0;  
            out = 0;  
        end else begin  
            q2 = q1;  
            q1 = in;  
            out = q2;  
        end  
    end  
end  
endmodule
```

```
module reg_non_blocking1 (  
    input clk, rst, in,  
    output reg out  
);  
    reg q, q2;  
    always @(posedge clk) begin  
        if (rst) begin  
            q2 <= 0;  
            q1 <= 0;  
            out <= 0;  
        end else begin  
            q2 <= q1;  
            q1 <= in;  
            out <= q2;  
        end  
    end  
end  
endmodule
```

```
module comb_blocking1 (  
    input a, b, c, clk,  
    output reg y  
);  
    always @(posedge clk) begin  
        x = a & b;  
        y = x | c;  
    end  
end  
endmodule
```

```
module comb_non_blocking1 (  
    input a, b, c, clk,  
    output reg y  
);  
    always @(posedge clk) begin  
        y <= x | c;  
        x <= a & b;  
    end  
end  
endmodule
```

Note: you can sketch the answer on a paper and add it to the assignment PDF

Submission Guidelines:

- The submitted file must be a PDF file.
- Name the file in the following format: StudentName _assignment3.pdf
- The PDF must include:
 - Verilog design codes, testbench and the do file for part 1
 - Verilog design codes for part 2 (Q3)
 - Sketches of the last question
 - Waveform snippets from QuestaSim showing test results of each question